

INDRAPRASTHA INSTITUTE *of*INFORMATION TECHNOLOGY DELHI

Department of Electronics & Communication Engineering

Embedded Logic Design

Midsem Lab Submission

SHIVAM SHUKLA 2022478


Source Code

Hierarchy



FSM Count file:

```
FSM_moore_1101.v
F:/ELD2023/Midsem_Lab_Exam_A/Midsem_Lab_Exam_A.srcs/sources_1/imports/new/FSM_moore_1101.v
          21
22
23 
module FSM_moore_1101(
24
         input Clk_pb,
25
         input Clear,
26
         output [8:0] FSM state,
         output reg Detect
27
28
         );
29
30
         parameter S0 = 9'b111110100, S1 = 9'b000000010, S2 = 9'b000001001, S3=9'b000010000;
31
         reg[8:0] present_state = S0;
32
         reg[8:0] next state;
33
34 ⊡
         always@(posedge Clk_pb or posedge Clear)
35 🖨
             begin
36 ⊖
                 if (Clear)
37
                     present state <= S0;
38
                 else
39 🖨
                     present_state <= next_state;
40 🖨
             end
41
42 🖨
         always@(*)
43 □
             begin
44 🗇
                 case (present state)
45
                     S0: next state = S1;
46
                     S1: next_state = S2;
                     S2: next state = S3;
48
                     S3: next state = S0;
49
                     default next state = S0;
50 🖨
                  endcase
51 🖨
              end
52
53 🖯
            always@(*)
54 🗇
                begin
55 ⊖
                     if (present_state == S0 || present_state == S2)
                                                                   99+
                                              Ħŧ
\blacksquare
```

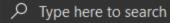


















```
FSM_moore_1101.v
F:/ELD2023/Midsem_Lab_Exam_A/Midsem_Lab_Exam_A.srcs/sources_1/imports/new/FSM_moore_1101.v
    parameter S0 = 9'b111110100, S1 = 9'b000000010, S2 = 9'b000001001, S3=9'b000010000;
30
31
        reg[8:0] present_state = S0;
32
        reg[8:0] next state;
33
34 🗇
        always@(posedge Clk_pb or posedge Clear)
35 🖨
            begin
36 ⊖
                if (Clear)
37
                   present_state <= S0;
38
39 🖨
                   present state <= next state;
40 🖨
            end
41
42 🗇
        always@(*)
43 □
            begin
44 🖨
                case (present state)
45
                   S0: next_state = S1;
46
                   S1: next_state = S2;
47 :
                   S2: next_state = S3;
48
                   S3: next_state = S0;
49 !
                   default next state = S0;
50 🗇
                 endcase
51 🖨
             end
52
53 🖨
           always@(*)
54 🗇
               begin
55 🖯
                    if (present state == S0 || present state == S2)
56
                       Detect = 1;
57
                   else
58 🖨
                       Detect = 0;
59 🗀
               end
60
61
           assign FSM_state = present_state;
62
63 ( endmodule
                                                  Ħŧ
Type here to search
```

 Clk_CMT / Clocking Wizard: (to get 6 MHZ 8.388*6/8=6.291 Frequency)




Clk CD file:

```
clk_div_rtl.v
F:/ELD2023/Midsem_Lab_Exam_A/Midsem_Lab_Exam_A.srcs/sources_1/imports/new/clk_div_rtl.v
10 // Target Devices:
11
   // Tool Versions:
12
   // Description:
13 ;
   11
   // Dependencies:
14
15
    11
16
    // Revision:
17
    // Revision 0.01 - File Created
18 // Additional Comments:
19 //
21
22
23 - module clk div rtl(
24
       input Clk 6M,
       output Clk_3Hz
25
26
27
28
29
       reg [20:0] Count_reg = 0;
                                   // 21 bits required because 6.291*10^6 / 2^21 = 2.86 Hz
30
       reg [20:0] Count_next;
31
32 ⊖
       always@(posedge Clk_6M)
33 🖯
34
              Count_reg <= Count_next;
35 🖨
           end
36
37 ⊡
        always@(*)
38 🖨
          begin
39 ;
              Count_next = Count_reg + 1;
40 🖨
41
42
         assign Clk_3Hz = Count_reg[20];
43 @ endmodule
44
```



top_counter file:

```
top_counter.v
F:/ELD2023/Midsem_Lab_Exam_A/Midsem_Lab_Exam_A.srcs/sources_1/imports/new/top_counter.v
    12
  // Description:
13 :
   //
14
  // Dependencies:
15
    11
   // Revision:
16
17 :
   // Revision 0.01 - File Created
18 :
   // Additional Comments:
19
21
22
23 
module top_counter(
24
      input Clk 100M,
25
       input Clr,
26
      output Detect,
27
      output [8:0] FSM_state
28
       );
29
30
      wire Clk 6M;
31
      wire Clk_3Hz;
32
33
      clk wiz 0 cml
34
35
       // Clock out ports
36
       .Clk_6M(Clk_6M),
                       // output Clk 8M
37
      // Clock in ports
       .Clk 100M(Clk 100M));
38
                            // input Clk 100M
39
    // INST TAG END ----- End INSTANTIATION Template -----
40
41
       clk_div_rtl cdl(.Clk_6M(Clk_6M),.Clk_3Hz(Clk_3Hz));
42
43
        FSM_moore_1101 f1(.Clk_pb(Clk_3Hz),.Clear(Clr),.FSM_state(FSM_state),.Detect(Detect));
44
45 @ endmodule
46
```

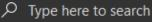


















Vio_Wrapper file:

 

Thank You